

# FPGA tutorial

## Lecture 10

13.01.2021

Jochen Steinmann

# Organisational

---



# ToDo:

---

- A. Create a RingBuffer, which can
- store 8x 8bit values
  - Two different clocks (read and write) each with its own enable
- B. Change the RingBuffer that it provides these features:
- Readout only, if write disabled
  - Output in the correct order (read pointer has to start from write pointer)
- Hint: Between read and write are some clock cycles of each clock.

Keep in mind:  
It is not possible to set variables in different processes.

- C. Start with a simple trigger module
- If reset, run = 1
  - If data is for one clockcycle above threshold run = 0 until reset

# Lecture 09a

```
entity RingBuffer is
  port(
    -- write
    i_sl_wrCLK      : in  std_logic;           -- clock
    i_sl_wrEN       : in  std_logic;           -- enable
    i_slv_wrdata    : in  std_logic_vector(7 downto 0); -- data input

    -- read
    i_sl_rdCLK      : in  std_logic;           -- clock
    i_sl_rdEN       : in  std_logic;           -- enable
    o_slv_rddata    : out std_logic_vector(7 downto 0) -- data output
  );
end RingBuffer;

-----

architecture behavior of RingBuffer is
  signal memory : slv8_array_t(7 downto 0) := (others=>(others=>'0'));

  -- read and write count 3 bit wide
  signal wrcnt  : unsigned(2 downto 0) := (others => '0');
  signal rdcnt  : unsigned(2 downto 0) := (others => '0');

begin

  process(i_sl_wrCLK)
  begin
    if rising_edge(i_sl_wrCLK) then
      if (i_sl_wrEN = '1') then
        memory( to_integer(wrcnt) ) <= i_slv_wrdata;

        wrcnt <= wrcnt + '1';
      end if;
    end if;
  end process;


  process(i_sl_rdCLK)
  begin
    if rising_edge(i_sl_rdCLK) then
      if (i_sl_rdEN = '1') then
        o_slv_rddata <= memory( to_integer(rdcnt) );

        rdcnt <= rdcnt + '1';
      end if;
    end if;
  end process;

end behavior;
```

# Lecture 09b

## Simulation output

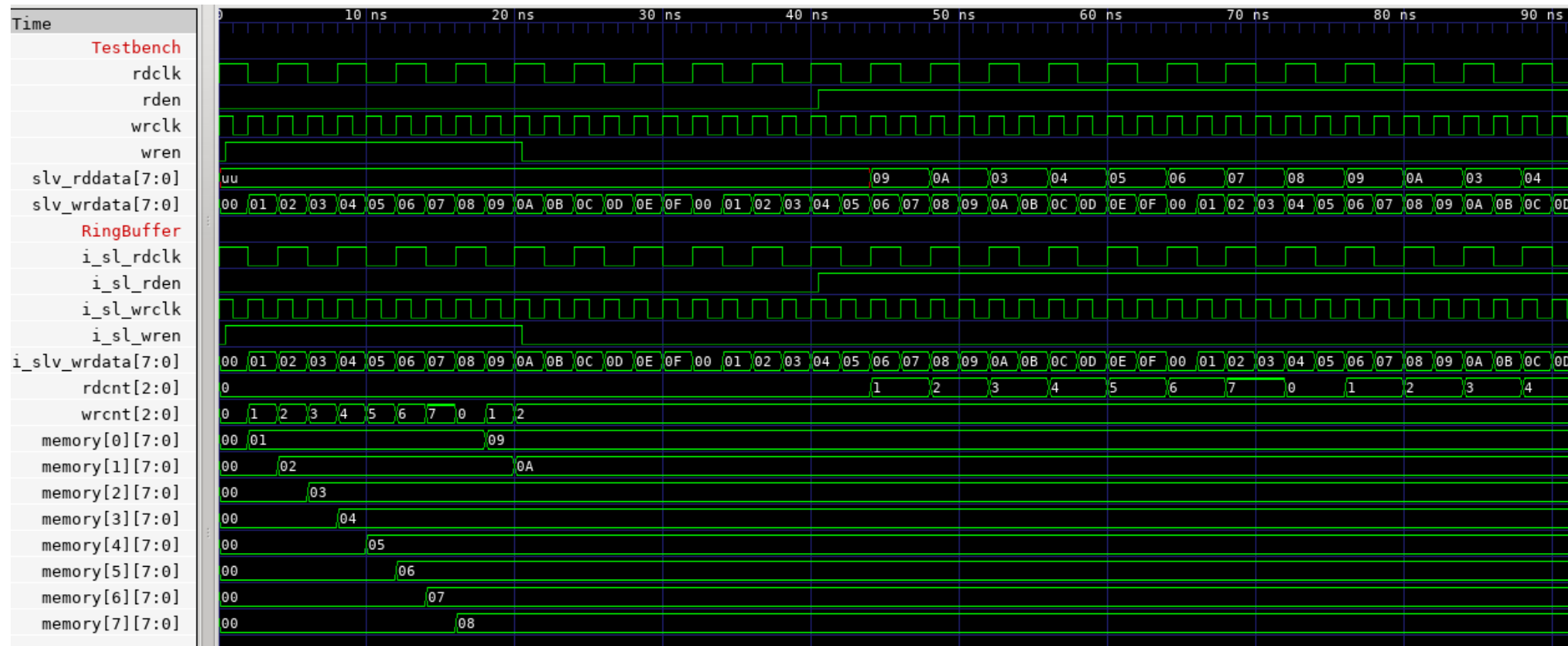

# Lecture 09b

## Keep the order of the data

```
architecture behavior of RingBuffer is
    signal memory : slv8_array_t(7 downto 0) := (others=>(others=>'0'));

    -- read and write count 3 bit wide
    signal wrcnt   : unsigned(2 downto 0) := (others => '0');
    signal rdcnt   : unsigned(2 downto 0) := (others => '0');

begin

    process(i_sl_wrCLK)
    begin
        if rising_edge(i_sl_wrCLK) then
            if (i_sl_wrEN = '1') then
                memory( to_integer(wrcnt) ) <= i_slv_wrdata;

                wrcnt <= wrcnt + '1';
            end if;
        end if;
    end process;


    process(i_sl_rdCLK)
    begin
        if rising_edge(i_sl_rdCLK) then
            if (i_sl_rdEN = '1') then
                o_slv_rddata <= memory( to_integer(rdcnt) ) ;

                rdcnt <= rdcnt + '1';
            else
                rdcnt <= wrcnt;
            end if;
        end if;
    end process;

end behavior;
```

Here we are setting the read counter to the write counter.  
This needs one clock cycle between writing and reading


## Simulation output

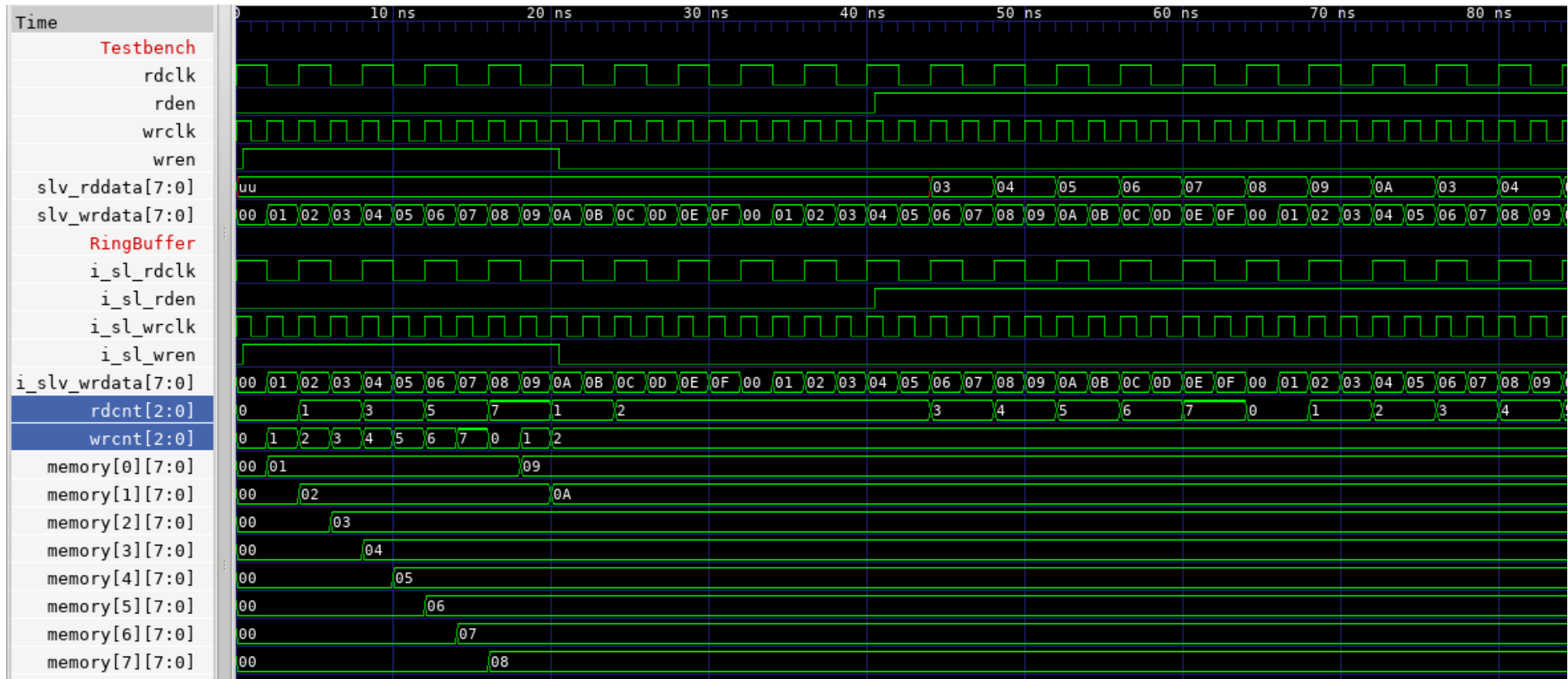



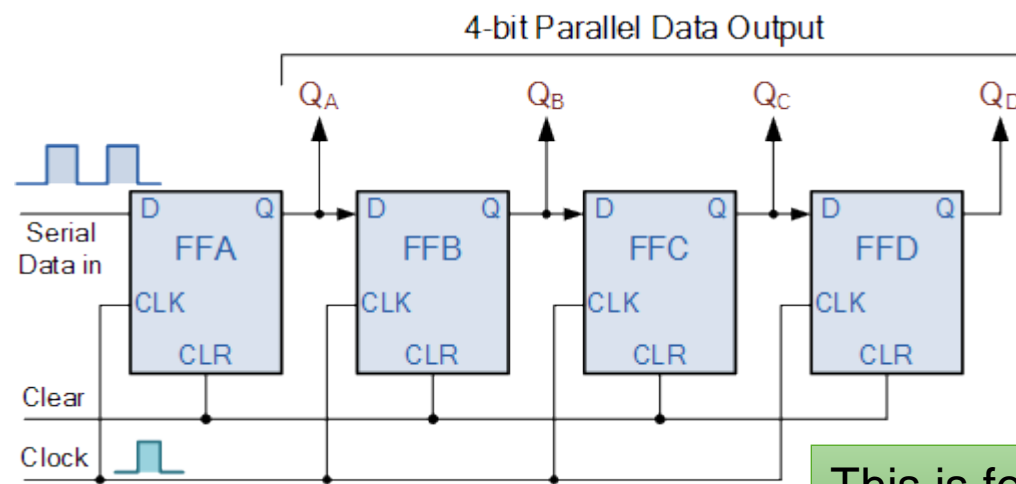
# Why using a read / write pointer

- The ringbuffer has the same functionality as our wide shift register
  - So where is the difference?
  - Assumption: we want to write 8 bits (data size)
  - Shift register looks like




This is for a single bit

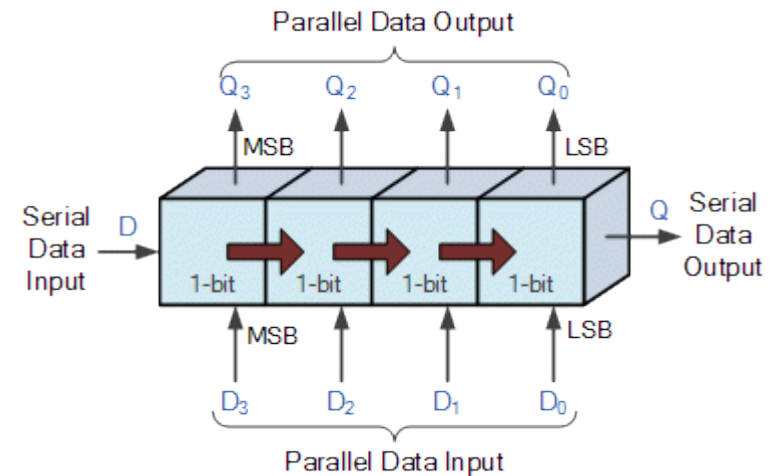

- If we store 8 x 8 bit, we have to update 64 bits in one clock cycle
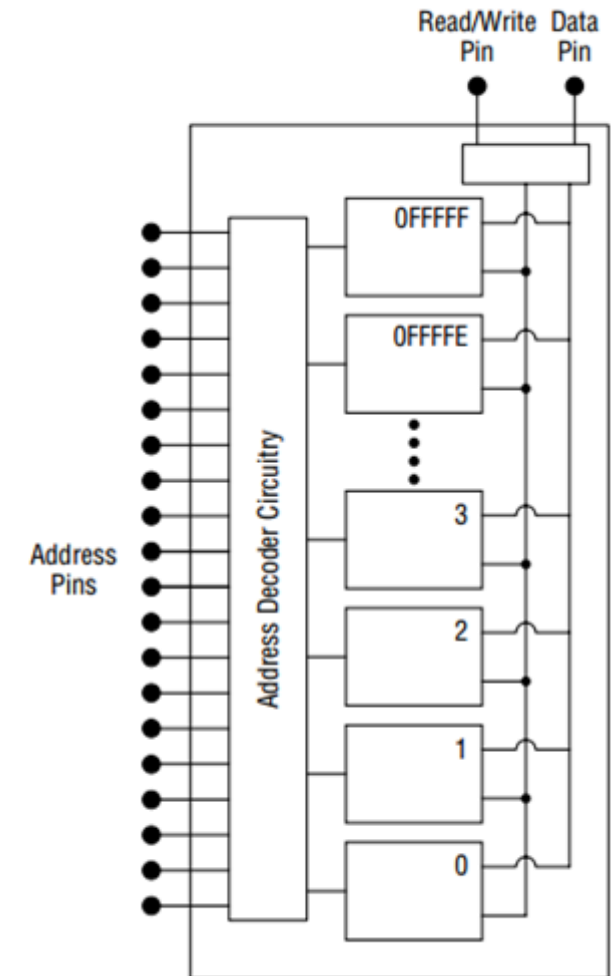
# Why using a read / write pointer II

- By using a write pointer, we can use different internal structures (e.g. RAM)
- Since we are just updating one 8 bit „data cell“, it's easier for the FPGA to write the data, less bit changes per clock cycle.



## Trigger module

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


-----

entity TriggerModule is
    port(
        i_sl_CLK      : in  std_logic;           -- clock
        i_sl_rst      : in  std_logic;           -- reset
        i_slv_data     : in  std_logic_vector(7 downto 0); -- data input
        i_slv_thr      : in  std_logic_vector(7 downto 0); -- threshold input
        o_sl_run       : out std_logic           -- run output
    );
end TriggerModule;

-----

architecture behavior of TriggerModule is
    signal run : std_logic := '0';
begin
    process(i_sl_CLK)
    begin
        if rising_edge(i_sl_CLK) then
            if (i_sl_rst = '1') then
                run <= '1';
            elsif ( unsigned(i_slv_data) > unsigned(i_slv_thr) ) then
                run <= '0';
            end if;
        end if;
        o_sl_run <= run;
    end process;
end behavior;
```

# Lecture 09c

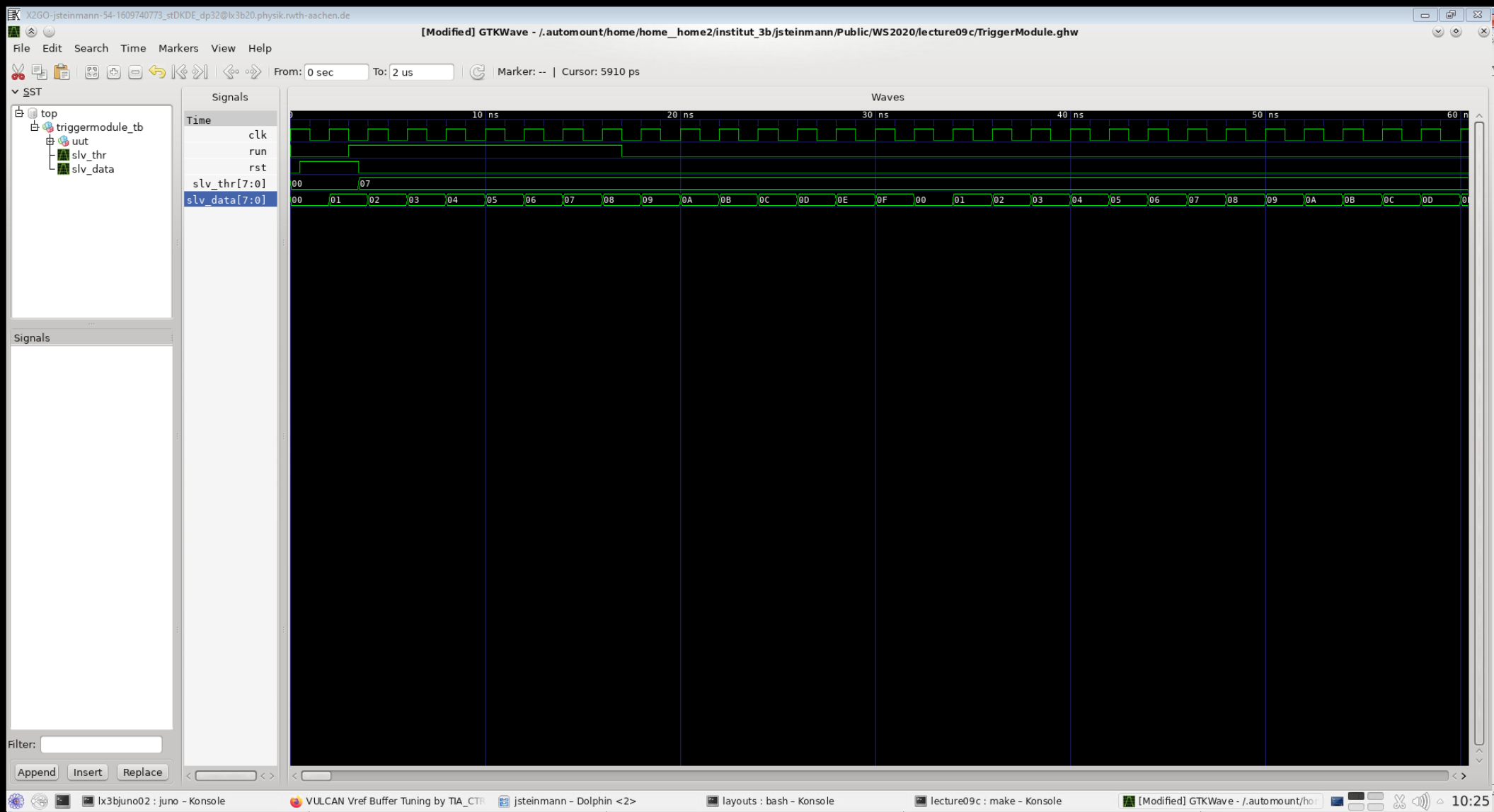

# NEW

# VHDL

# When / Else statement

---

**a**

- Sometimes, it is required to set a signal independent of a clock
- e.g.
  - Set signal / output empty to ,1' if cnt is zero, set it to zero otherwise

```
empty <= '1' when ( cnt = x"0" ) else '0';
```


# Storing data and analysing it later



## Many different clocks


- External signals
- Clocks & data from ADCs
- Local clocks
- Generated clocks
- Each clock has to be treated as a separate clock, even, if the frequency is the same

# Clocks in a real FPGA based readout

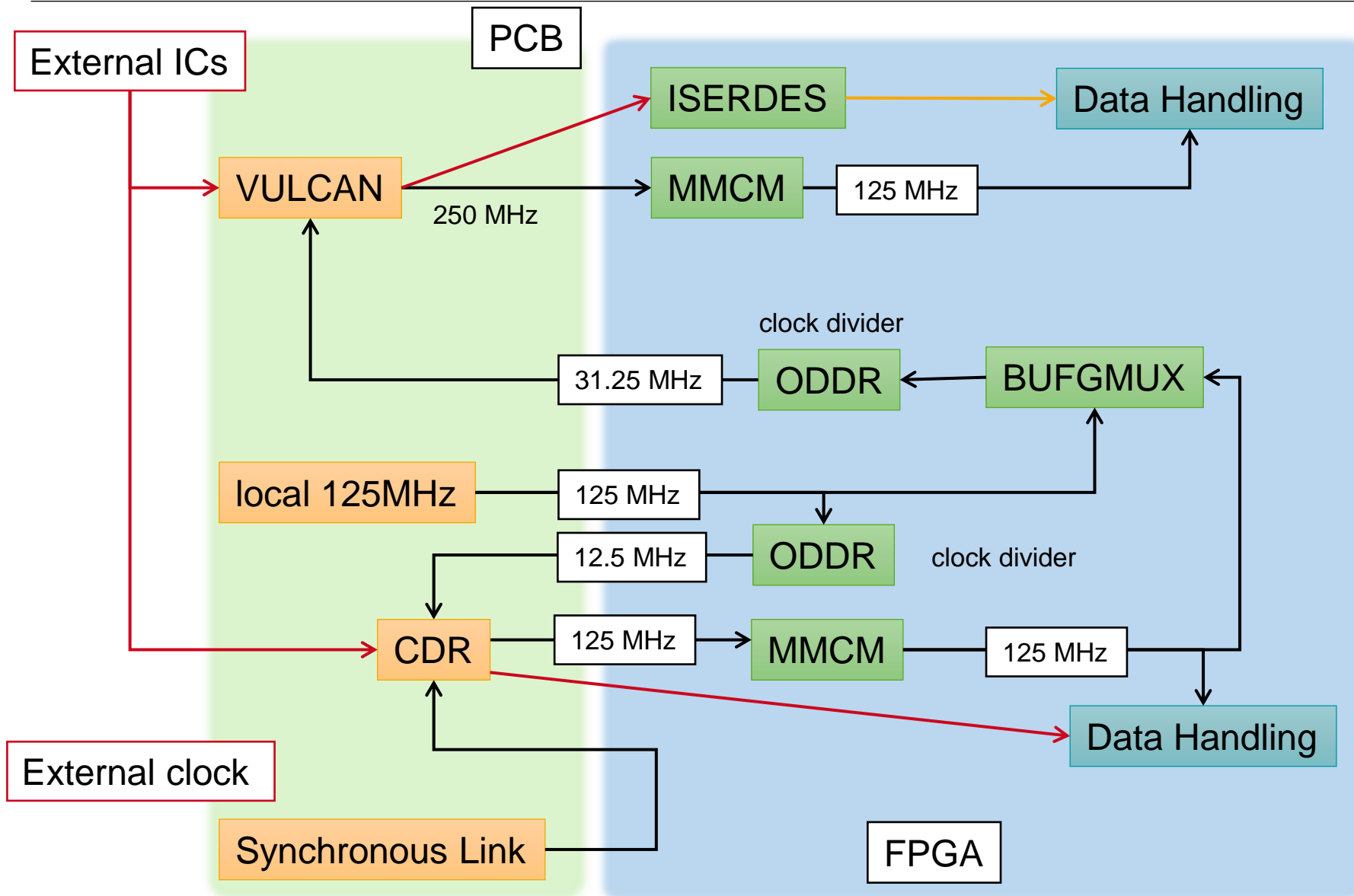

# How to transmit data between different clocks


## Clock domain crossing

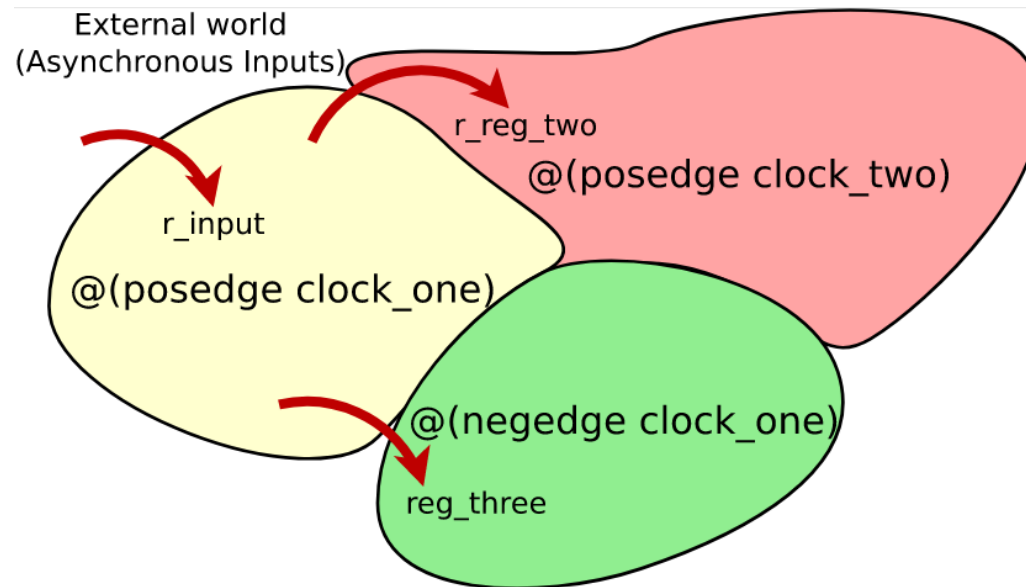

- Assumption:
  - we have one “sampling” event, which generates the data
  - additionally we have one “readout” event, which displays the data
  - both events must not be clocks, they can also be events generated by buttons, etc.


# Sketch

---

 


- We want to keep the order of the data
    - first input element should appear at the output as the first element
- FIFO** → First In First Out

# Using a FiFo

 

# FIFO in real life

 



# FIFO in real life

---



[ssi-schaefer.de/](http://ssi-schaefer.de/)

- Synchronous FiFos

same clock for read and write

- read and write clock is the same
  - Data storage
  - Protocol handling


- Asynchronous FiFos

- read and write clock can be different
- clock domain crossing
  - data transfer from one clock region to another

- If you want to use complex FIFOs
  - There is the possibility to use tools from the FPGA vendor to create FiFo
- But: This is an educational course, so we are going to build our own FiFo.
 
# How is a FiFo working?

- Simple FiFo:
  - using ring buffer
  - read “pointer”
  - write “pointer”



# How to input data to the FiFo

## Writing to FiFo:

if not full

write data to position given by write poi  
increase write pointer by 1


## Reading from FiFo:

if not empty

read data from position given by  
read pointer  
increase read pointer by 1
 
## Bookkeeping:

count number of elements currently stored in  
Fifo → count number of read and writes




**Not simply subtract read and write pointer this might result in trouble!**

# Our Verilog FiFo

---


- We are building a synchronous FIFO
  - Read and Write Clock is the same
  - Data transfer on rising edge
- Storage Width => width of input and output bus
- Storage Depth => width of address bus
- Read enable
- Write enable
- Full Flag
- Empty Flag

# FIFO in electronics

 

# Synchronous FiFo

---

 



# Synchronous FiFo

---

- First start with the implementation of the FiFo
- Hint: when operating a FiFo, we can identify three blocks
  - input (input clock)
    - Write pointer
  - output (output clock)
    - Read pointer
  - bookkeeping (input & output clock)
    - Count elements

# ToDo for today

---

## Lecture 10

### A. Implement a synchronous FiFo

- Status outputs:
  - Full
  - Empty
- Control inputs:
  - Reset
  - Read enable
  - Write enable

### B. Implement a asynchronous FiFo

- Same inputs and outputs as above
- BUT: a additional read / write clock
- **Note:** The full and empty flags are not that trivial
- Think about why this is not trivial, and about a possible way to solve this.

# Thank you!