

FPGA tutorial

Lecture 11

20.01.2021

Jochen Steinmann

Organisational



ToDo from last time

Lecture 10

A. Implement a synchronous FiFo

- Status outputs:
 - Full
 - Empty
- Control inputs:
 - Reset
 - Read enable
 - Write enable

B. Implement a asynchronous FiFo

- Same inputs and outputs as above
- BUT: a additional read / write clock
- **Note:** The full and empty flags are not that trivial
- Think about why this is not trivial, and about a possible way to solve this.

Synchronous FiFo (Simulation)

```
architecture behavior of SyncFiFo is
    signal memory : slv8_array_t(7 downto 0) := (others=>(others=>'0'));    -- storage

    -- read and write count 3 bit wide
    signal wrcnt : unsigned(2 downto 0) := (others => '0');    -- write pointer
    signal rdcnt : unsigned(2 downto 0) := (others => '0');    -- read pointer

    signal cnt : unsigned(3 downto 0) := (others => '0');    -- how many elements are in the FiFo?

    signal full : std_logic := '0';
    signal empty : std_logic := '0';
begin

    process(i_sl_CLK)    -- read and write
    begin
        if rising_edge(i_sl_CLK) then
            if ( i_sl_reset = '1' ) then
                -- reset read and write counter
                rdcnt <= (others => '0');
                wrcnt <= (others => '0');


                cnt <= (others => '0');    -- reset counter
            else
                if (i_sl_wrEN = '1' and full = '0') then    -- write only, when not full
                    memory( to_integer(wrcnt) ) <= i_slv_wrdata;
                    wrcnt <= wrcnt + '1';
                end if;

                if (i_sl_rdEN = '1' and empty = '0') then    -- read only, when not empty
                    o_slv_rddata <= memory( to_integer(rdcnt) ) ;
                    rdcnt <= rdcnt + '1';
                end if;

                -- bookkeeping
                if (i_sl_wrEN = '1' and i_sl_rdEN = '0' and full = '0') then    -- we are adding elements
                    cnt <= cnt + '1';
                elsif (i_sl_wrEN = '0' and i_sl_rdEN = '1' and empty = '0') then    -- we are removing elements
                    cnt <= cnt - '1';
                end if;
            end if;
        end if;
    end process;

    empty <= '1' when ( cnt = x"0" ) else '0';
    full <= '1' when ( cnt = x"8" ) else '0';
end;
```

Synchronous FiFo (Simulation)

 

Asynchronous FiFo

```
architecture behavior of SyncFiFo is
    signal memory : slv8_array_t(7 downto 0) := (others=>(others=>'0'));    -- storage

    -- read and write count 3 bit wide
    signal wrcnt : unsigned(2 downto 0) := (others => '0');    -- write pointer
    signal rdcnt : unsigned(2 downto 0) := (others => '0');    -- read pointer

    signal cnt : unsigned(3 downto 0) := (others => '0');    -- how many elements are in the FiFo?

    signal full : std_logic := '0';
    signal empty : std_logic := '0';
begin

    empty <= '1' when ( wrcnt = rdcnt ) else '0';
    full <= '1' when ( rdcnt = wrcnt + '1' ) else '0';

    o_sl_empty <= empty;
    o_sl_full <= full;


    process(i_sl_wCLK)    -- write
    begin
        if rising_edge(i_sl_wCLK) then
            if ( i_sl_reset = '1' ) then
                wrcnt <= (others => '0');
            else
                if (i_sl_wrEN = '1' and full = '0') then    -- write only, when not full
                    memory( to_integer(wrcnt) ) <= i_slv_wrdata;
                    wrcnt <= wrcnt + '1';
                end if;
            end if;
        end if;
    end process;

    process(i_sl_rCLK)    -- read
    begin
        if rising_edge(i_sl_rCLK) then
            if ( i_sl_reset = '1' ) then
                rdcnt <= (others => '0');
            else
                if (i_sl_rdEN = '1' and empty = '0') then    -- read only, when not empty
                    o_slv_rddata <= memory( to_integer(rdcnt) );
                    rdcnt <= rdcnt + '1';
                end if;
            end if;
        end if;
    end process;


end behavior;
```

Full / Empty

 - Using the features of the memory
 - Storing 8 elements => 3bit address width
- Keep in mind:
 - $15 + 1 = 0$ (for a 4 bit unsigned)
 - $7 + 1 = 0$ (for a 3 bit unsigned)



Asynchronous FiFo (Simulation)

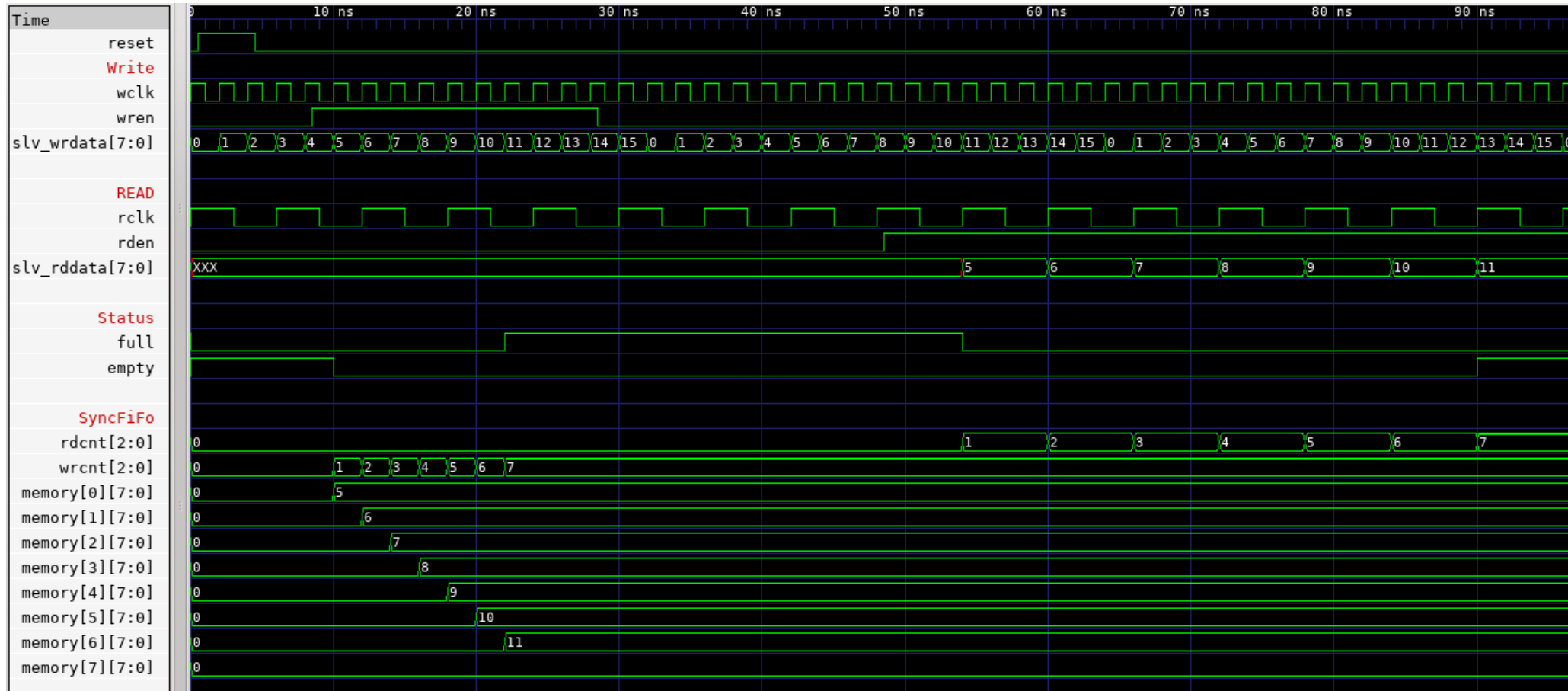

Drawbacks of this method?

What do you think?

NEW

VHDL

Type definition enum

- Synthesis tools map enumerations onto a suitable bit pattern automatically

```
architecture EXAMPLE of ENUMERATION is
  type T_STATE is
    (RESET, START, EXECUTE, FINISH);

  signal CURRENT_STATE : T_STATE;
  signal NEXT_STATE   : T_STATE;
  signal TWO_BIT_VEC  : bit_vector(1 downto 0);

begin

  -- valid signal assignments
  NEXT_STATE    <= CURRENT_STATE;
  CURRENT_STATE <= RESET;

  -- invalid signal assignments
  CURRENT_STATE <= "00";
  CURRENT_STATE <= TWO_BIT_VEC;

end EXAMPLE;
```

Finite State Machines

Doing different tasks




Finite State Machines

- Until now only „programs“ with always the same behaviour
- Sometimes, it is necessary to react on different situations
 - If triggered – read out the detector
 - If done – wait for next trigger and do nothing
- Useful:
 - Finite State Machines
- In this course: No complete introduction on FSM

In General

 - FSM always needs an event to change state!
- **very simple model**
 - Two States (ON / OFF)
 - Two Events (DOWN / UP)
- Each state consists of:
 - Input action
 - Action done, when entering the state
 - State action
 - Action done, when being inside the state
 - Output action
 - Action done, when leaving the state



ON

IA: switch light on
SA: keep light on
OA: nothing

OFF

IA: switch light off
SA: keep light off
OA: nothing

Definition of an Event

- Event causes FSM to change the state
 - Can be clock, buttons or other trigger information
 - But also more complex structures

Definition of a state

- Input action
 - Output, when entering the state
- Output action
 - Output when leaving the state
- Action during the state


Advantage of FSMs

- Why FSMs are nice:
 - For given events, they always behave the same
 - If their state is known, you know what they are doing
- Usage of FSMs
 - Decoding of protocols
 - start – data – stop
 - Different operation modes
 - Initialisation
 - Run
 - Shutdown
 - User interactions
 - Menu structure

Planning of a FSM

- State and transition table is very helpful
- States and events and their actions are listed in the table


		from		
		State A	State B	State C
at	Event A	State B		
	Event B		State C	State B
	Event C			State A

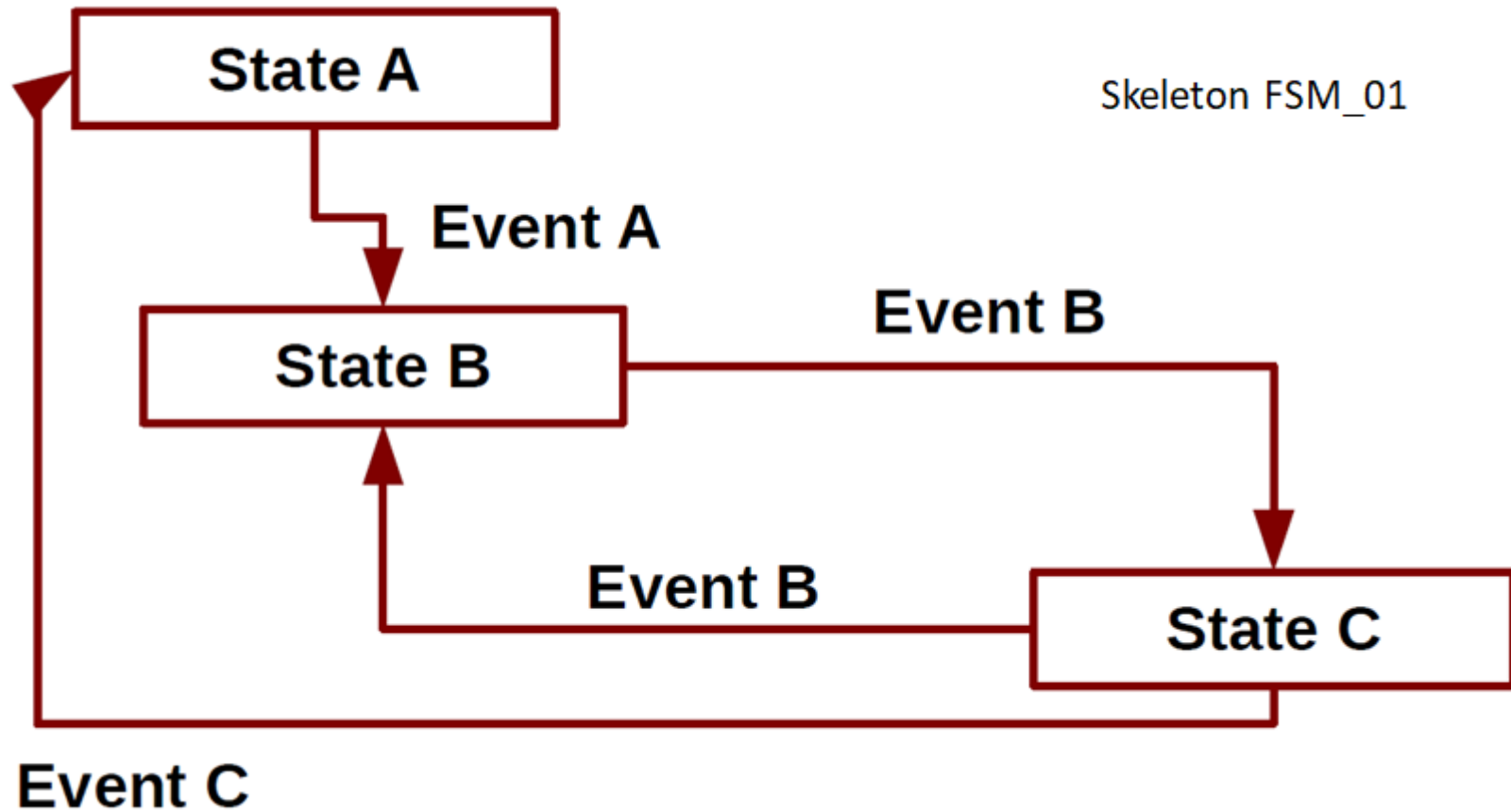

Three blocks State machines


Some special kind of FSM implementation

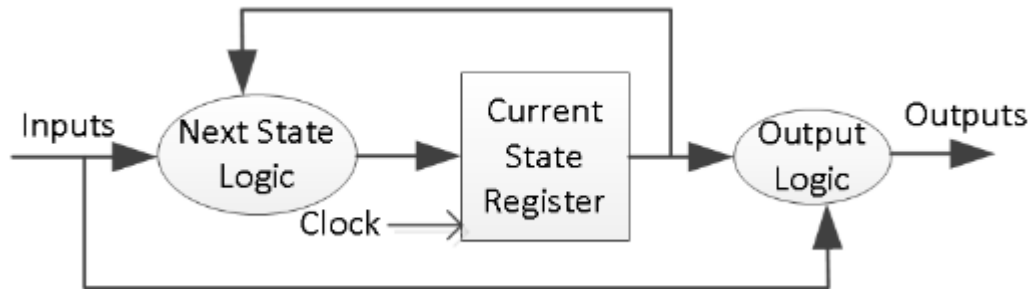- Three processes handling different things



Mealy FSM:

Outputs depend on states + inputs

 

Moore FSM:

Outputs depend on states

Process 1

Handling the next state

```
type state_type is (S0, S1);  
signal state, next_state : state_type;  
  
SYNC_PROC : process (clk) begin  
    if rising_edge(clk) then  
        if (reset = '1') then  
            state <= S0;  
        else  
            state <= next_state;  
        end if;  
    end if;  
end process;
```

Process 2

Preparing the next state

```
NEXT_STATE_DECODE : process (state, x) begin
    next_state <= S0;
    case (state) is
        when S0 =>
            if (x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
        end case;
    end process;
```


Process 3

Handling the output

```
OUTPUT_DECODE : process (state, x) begin
    parity <= '0';
    case (state) is
        when S0 =>
            if (x = '1') then
                parity <= '1';
            end if;
        when S1 =>
            if (x = '0') then
                parity <= '1';
            end if;
        when others =>
            parity <= '0';
        end case;
    end process;
```


ToDo Lecture 11

- A. Implement the three process **Marley** FSM presented in these slides
- B. Design a sequence detector implementing a Mealy state machine using three blocks.

The Mealy state machine has one input (ain) and one output (yout).

The output yout is 1 if and only if the total number of 1s received is divisible by 3 (hint: 0 is inclusive, however, reset cycle(s) do not count as 0- see in simulation waveform time=200).

 Develop a testbench and verify the model through a behavioral simulation.




ToDo Lecture 11

C. Implement a FSM outputting the Fibonacci numbers Reminder: $0 - 1 - 1 - 2 - 3 - 5 - \dots - (n-1 + n-2)$

- States:
 - 1 init
 - 2 output 0
 - 3 output 1
 - 4 create Fibonacci number
 - 5 keep output
 - 5 can be ignored depending on your implementation
- Events:
 - 1: CLK = btnD
 - 2: en
 - 3: Reset

There are various ways, how to approach this.

 Please let me know, whether you completed C!



Thank you!