

# FPGA tutorial

## Lecture 12

27.01.2021

Jochen Steinmann

# Organisational

---

# Discussion of Evaluation

---

# How does the exam look like?

---

I uploaded you a previous exam.

## Note:

1. I changed the language from VERILOG to VHDL of the course.  
There are language specific differences.
2. Previous courses used real hardware, this time „just“ simulation.  
Topics might be different.




# ToDo Lecture 11

- A. Implement the three process **Marley** FSM presented in these slides
- B. Design a sequence detector implementing a Mealy state machine using three blocks.

The Mealy state machine has one input (ain) and one output (yout).

The output yout is 1 if and only if the total number of 1s received is divisible by 3 (hint: 0 is inclusive, however, reset cycle(s) do not count as 0- see in simulation waveform time=200).

 Develop a testbench and verify the model through a behavioral simulation.




# ToDo Lecture 11

## C. Implement a FSM outputting the Fibonacci numbers Reminder: $0 - 1 - 1 - 2 - 3 - 5 - \dots - (n-1 + n-2)$

- States:
  - 1 init
  - 2 output 0
  - 3 output 1
  - 4 create Fibonacci number
  - 5 keep output
    - 5 can be ignored depending on your implementation
- Events:
  - 1: CLK = btnD
  - 2: en
  - 3: Reset

There are various ways, how to approach this.

 Please let me know, whether you completed C!




There is time to continue this exercise today...

# Lecture 11 a

```
SYNC_PROC : process (i_sl_clk) begin
    if rising_edge(i_sl_clk) then
        if (i_sl_reset = '1') then
            state <= S0;
        else
            state <= next_state;
        end if;
    end if;
end process;
```

```
OUTPUT_DECODE : process (state, i_sl_x) begin
    o_sl_parity <= '0';
    case (state) is
        when S0 =>
            if (i_sl_x = '1') then
                o_sl_parity <= '1';
            end if;
        when S1 =>
            if (i_sl_x = '0') then
                o_sl_parity <= '1';
            end if;
        when others =>
            o_sl_parity <= '0';
        end case;
    end process;
```

```
NEXT_STATE_DECODE : process (state, i_sl_x) begin
    next_state <= S0;
    case (state) is
        when S0 =>
            if (i_sl_x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (i_sl_x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
        end case;
    end process;
```

 



# Lecture 11 b

architecture behavior of FSM\_02 is

```
type state_type is (S0, S1, S2, S3);
signal state, next_state : state_type;


begin

SYNC_PROC : process (i_sl_clk) begin
    if rising_edge(i_sl_clk) then
        if (i_sl_reset = '1') then
            state <= S0;
        else
            state <= next_state;
        end if;
    end if;
end process;

OUTPUT_DECODE : process (state, i_sl_x) begin
    o_sl_parity <= '0';
    case (state) is
        when S3 =>
            o_sl_parity <= '1';
        when others =>
            o_sl_parity <= '0';
    end case;
end process;
```

```
NEXT_STATE_DECODE : process (state, i_sl_x) begin
    next_state <= S0;
    case (state) is
        when S0 =>
            if (i_sl_x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (i_sl_x = '1') then
                next_state <= S2;
            end if;
        when S2 =>
            if (i_sl_x = '1') then
                next_state <= S3;
            end if;
        when S3 =>
            if (i_sl_x = '1') then
                next_state <= S0;
            end if;
        when others =>
            next_state <= S0;
    end case;
end process;
```

# Lecture 11 b

 

**NEW**

# VHDL

# Using a component

---

- In the past, we always used  
COMPONENT test

UUT : test  
PORT MAP

- There is an alternative way of doing this

UUT : entity work.test(behavior) <- this is using the behavior architecture of  
module test, which is the library work  
(our default work space)

Useful, if you have many inputs / outputs

## How to reset?

- Basically there are two ways of how to reset?
  - Reset if reset signal is = 1
  - Reset if reset signal is = 0 (sometimes also called non reset / nReset / nRST)
- Both are doing their job
- Why is resetting on 0 is a smart way?

# Not reset?


---

- When to reset?
  - Power on, to get a well defines state
    - Note: setting a default value for signals / variables does just work in the simulation.
    - Inside the FPGA you might end up with a strange behavior, if not using reset.
  - Any situation, which requires a reset...


# Not reset!
 
## Power on reset by just two additional components

Acceptable TTL gate  
input signal levels



 Acceptable TTL gate  
output signal levels




Most of the ICs used in electronics are using  
a non-reset.

It is easier to use.

Inside the FPGA it does not matter, which type of  
reset you are using

Figure 3-1. Recommended Reset Pin connection.

 



# Thinking in states...

---

- Example: Exercise 11B
  - The output yout is 1 if and only if the total number of 1s received is divisible by 3 (hint: 0 is inclusive, however, reset cycle(s) do not count as 0- see in simulation waveform time=200).
- Which states can we identify?
  - a) Zero ones
  - b) Single one
  - c) Double one
  - d) Triple one
- Which transitions are needed?
  - A -> B -> C -> D -> A
- When to do the transition?
  - If input x = 1

# Finite State Machines

Doing different tasks



## Finite State Machine


- The state changing part...

```
process(Clk) is
begin
    if rising_edge(Clk) then
        if nRst = '0' then
            State <= <reset_state>;
        else
            case State is
                when <state_name> => <set_outputs_for_this_state_here>
                    if <state_change_condition_is_true> then
                        State <= <next_state_name>;
                    end if;
                ...
            end case;
        end if;
    end if;
end process;
```


# Continuation of FSM

## Situation given

- Intersection with traffic lights

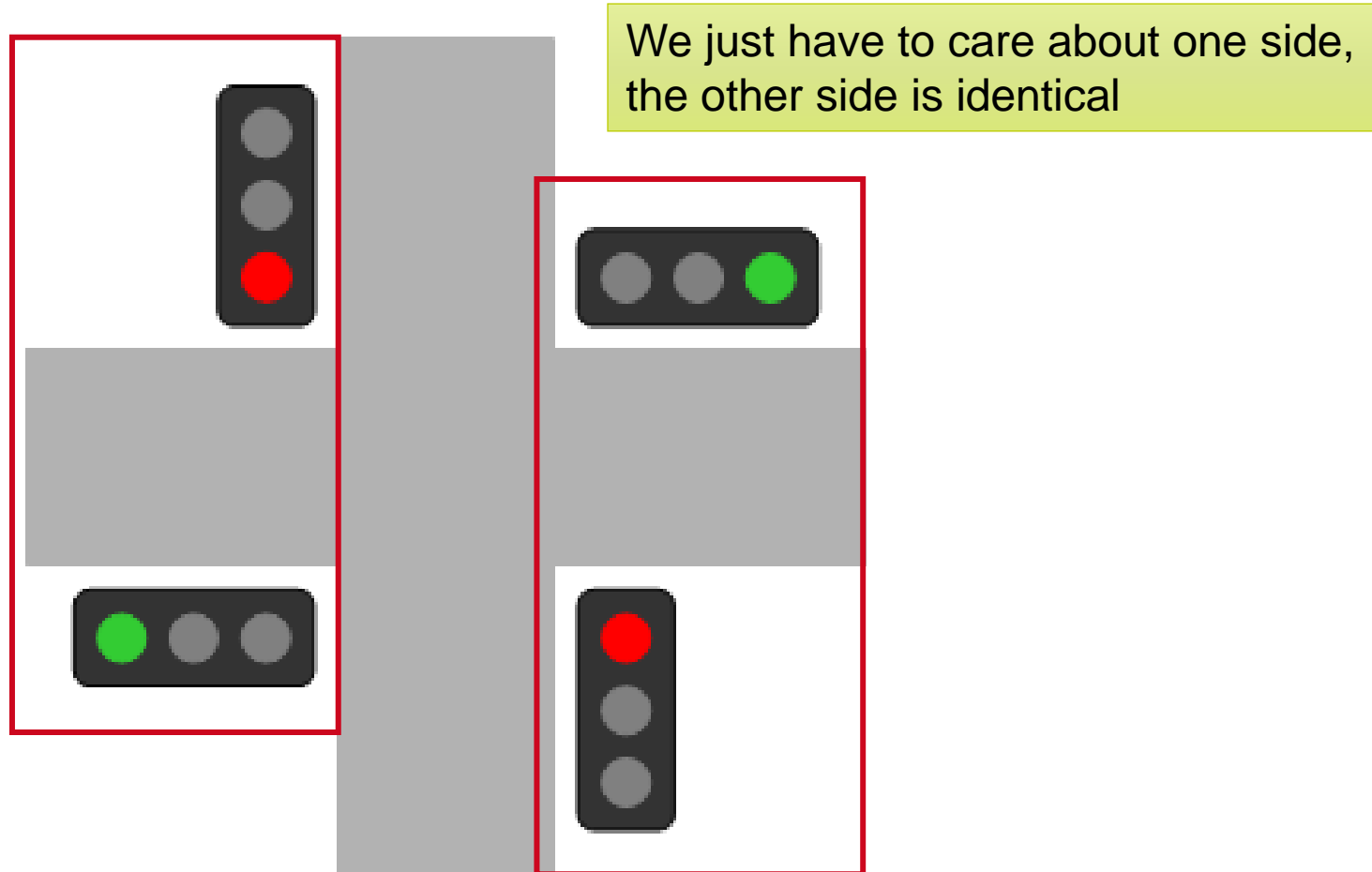

# How does the intersection behave?

 

## Intersection:

All red – one directions gets green – All red – next direction gets green.

# Designing the FSM

---

- Think about which states can you observe / think of
- Which transitions are needed?
- Draw a diagram of the FSM (this helps implementing the states)
- Implement the FSM
- Do you have any idea how to increase the length of the green state?

# ToDo Lecture 12

---

- A. Implement the intersections FSM
- B. Continue implementation of last weeks Fibonacci FSM

# Few words regarding the testbench skeleton

```
-- Testbench sequence
process is
begin
    wait until rising_edge(Clk);    -- wait for rising edge
    wait until rising_edge(Clk);    --

    -- Take the DUT out of reset
    nRst <= '1';

    wait;    -- wait forever
end process;
```





# Thank you!